

```
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%  
%%% Hyeongmeen Baik  
%%% ECE412 Power Electronics  
%%% HW 3
```

### Q3

```
clc;  
clear;  
Vo_min = 5
```

```
Vo_min = 5
```

```
Vo_max = 20
```

```
Vo_max = 20
```

```
IESR = 10
```

```
IESR = 10
```

```
RESR = 0.05
```

```
RESR = 0.0500
```

```
Vin = 12
```

```
Vin = 12
```

```
%%% Vo_min case  
D1 = (IESR*RESR+Vo_min)/(Vo_min+Vin)
```

```
D1 = 0.3235
```

```
Io1 = IESR-D1*IESR
```

```
Io1 = 6.7647
```

```
Iin1 = D1*IESR
```

```
Iin1 = 3.2353
```

```
Pin1 = Vin*Iin1
```

```
Pin1 = 38.8235
```

```
Po1 = Io1*Vo_min
```

```
Po1 = 33.8235
```

```
Rload1 = Vo_min/Io1
```

$$R_{load1} = 0.7391$$

$$n1 = P_{o1}/P_{in1} \times 100$$

$$n1 = 87.1212$$

%%% Vo\_max case

$$D2 = (I_{ESR} \times R_{ESR} + V_{o\_max}) / (V_{o\_max} + V_{in})$$

$$D2 = 0.6406$$

$$I_{o2} = I_{ESR} - D2 \times I_{ESR}$$

$$I_{o2} = 3.5938$$

$$I_{in2} = D2 \times I_{ESR}$$

$$I_{in2} = 6.4063$$

$$P_{in2} = V_{in} \times I_{in2}$$

$$P_{in2} = 76.8750$$

$$P_{o2} = I_{o2} \times V_{o\_max}$$

$$P_{o2} = 71.8750$$

$$R_{load2} = V_{o\_max} / I_{o2}$$

$$R_{load2} = 5.5652$$

$$n2 = P_{o2} / P_{in2} \times 100$$

$$n2 = 93.4959$$

$$P_{ESR} = I_{ESR}^2 \times R_{ESR}$$

$$P_{ESR} = 5$$

## Q4

%%% Vo\_min case

$$V_{s1} = (1 - D1) \times (V_{in} + V_{o\_min})$$

$$V_{s1} = 11.5000$$

$$V_{sRMS1} = \sqrt{(1 - D1) \times (V_{in} + V_{o\_min})}$$

$$V_{sRMS1} = 13.9821$$

$$V_{sPeak1} = V_{in} + V_{o\_min}$$

VsPeak1 = 17

$V_{d1} = D1 \cdot (V_{o\_min} + V_{in})$

Vd1 = 5.5000

$V_{dRMS1} = \sqrt{D1} \cdot (V_{o\_min} + V_{in})$

VdRMS1 = 9.6695

$V_{dpeak1} = V_{o\_min} + V_{in}$

Vdpeak1 = 17

%%% Vo\_max case

$V_{s2} = (1 - D2) \cdot (V_{in} + V_{o\_max})$

Vs2 = 11.5000

$V_{sRMS2} = \sqrt{1 - D2} \cdot (V_{in} + V_{o\_max})$

VsRMS2 = 19.1833

$V_{sPeak2} = V_{in} + V_{o\_max}$

VsPeak2 = 32

$V_{d2} = D2 \cdot (V_{o\_max} + V_{in})$

Vd2 = 20.5000

$V_{dRMS2} = \sqrt{D2} \cdot (V_{o\_max} + V_{in})$

VdRMS2 = 25.6125

$V_{dpeak2} = V_{o\_max} + V_{in}$

Vdpeak2 = 32

## Q5

```
clc;
clear;
Vin = 12;
Vo = 20;
D_boost = (Vo - Vin) / Vo
```

D\_boost = 0.4000

$D_{buckboost} = V_o / (V_{in} + V_o)$

D\_buckboost = 0.6250

```
deliL = 100e-3
```

```
deliL = 0.1000
```

```
fs = 50e3
```

```
fs = 50000
```

```
Ts = 1/fs
```

```
Ts = 2.0000e-05
```

```
L_boost = Vin*D_boost*Ts/deliL
```

```
L_boost = 9.6000e-04
```

```
L_buckboost = Vin*D_buckboost*Ts/deliL
```

```
L_buckboost = 0.0015
```

```
%%% ideal case
```

```
Vsbuckboost = (1-D_buckboost)*(Vin+Vo)
```

```
Vsbuckboost = 12
```

```
VsbuckboostRMS = sqrt(1-D_buckboost)*(Vin+Vo)
```

```
VsbuckboostRMS = 19.5959
```

```
VsbuckboostPeak = (Vin+Vo)
```

```
VsbuckboostPeak = 32
```

```
Vdbuckboost = D_buckboost*(Vo+Vin)
```

```
Vdbuckboost = 20
```

```
VdbuckboostRMS = sqrt(D_buckboost)*(Vo+Vin)
```

```
VdbuckboostRMS = 25.2982
```

```
VdbuckboostPeak = Vo+Vin
```

```
VdbuckboostPeak = 32
```

```
%%% ideal case
```

```
Vsboost = (1-D_boost)*(Vo)
```

```
Vsboost = 12
```

```
VsboostRMS = sqrt(1-D_boost)*(Vo)
```

```
VsboostRMS = 15.4919
```

```
VsboostPeak = (Vo)
```

```
VsboostPeak = 20
```

```
Vdboost = D_buckboost*(Vo-Vin)
```

```
Vdboost = 5
```

```
VdboostRMS = sqrt(D_buckboost)*(Vo-Vin)
```

```
VdboostRMS = 6.3246
```

```
VdboostPeak = Vo-Vin
```

```
VdboostPeak = 8
```

```
%%% Considering ESR for boost converter
```

```
Vin = 12
```

```
Vo= 20
```

```
RESR = 0.05
```

```
syms Iin
```

```
eqn=Vin-Iin*RESR == Vo/Iin*20/5.5652
```

```
S=solve(eqn)
```

```
Iin = double(S(1,1))
```

```
D = 1-3.5938/Iin
```